

Calculator project introduction

Kevin Wang


kevin.wang@auckland.ac.nz

303.154


2016

Simple calculator


- Project summary: a simple calculator that
 - Accepts and stores up to two digits integer input (value range?) for both operands
 - Performs
 - Two operands op: addition, subtraction, multiplication, or division on the operands
 - For the result of division, display integer quotient and remainder
 - Display the entered operands and computed results as integer values on the 7-segment displays
 - Keys on the keypad are used for entering digits and operations

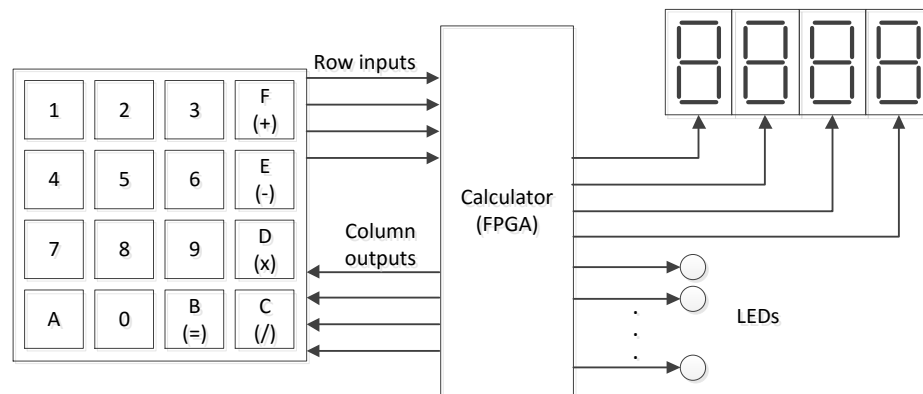


Simple calculator

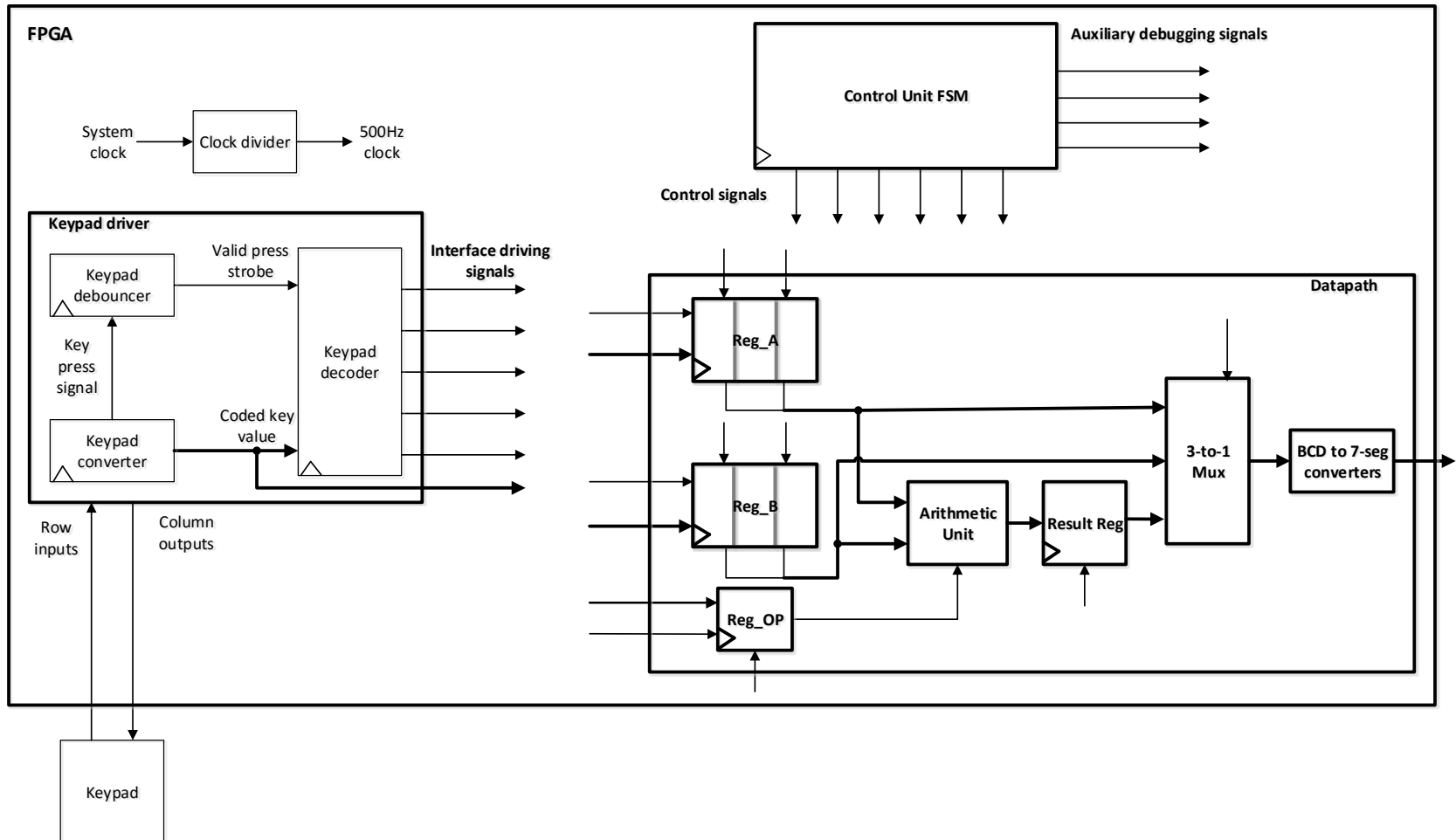

Simple calculator in reality

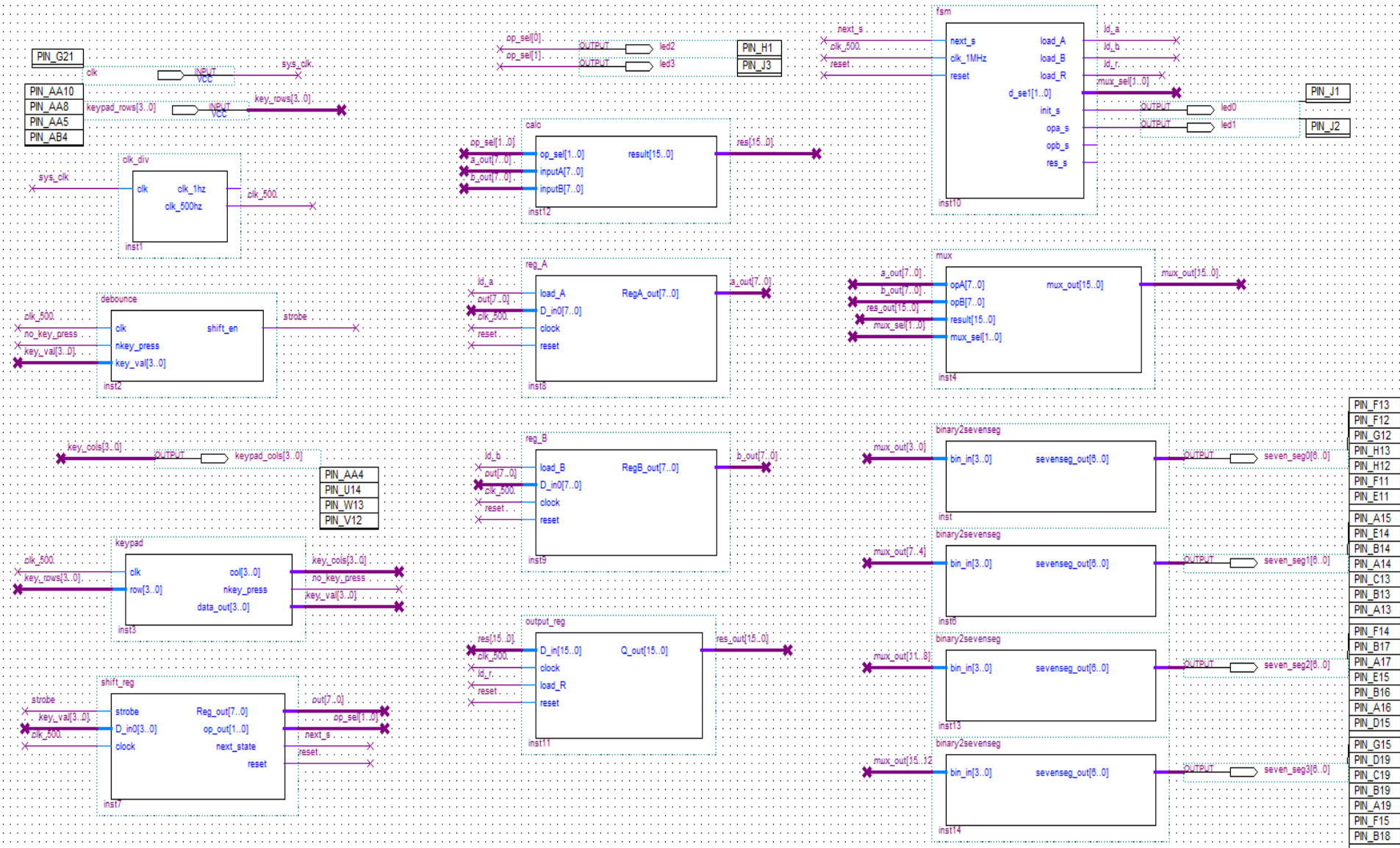


Matrix keypad

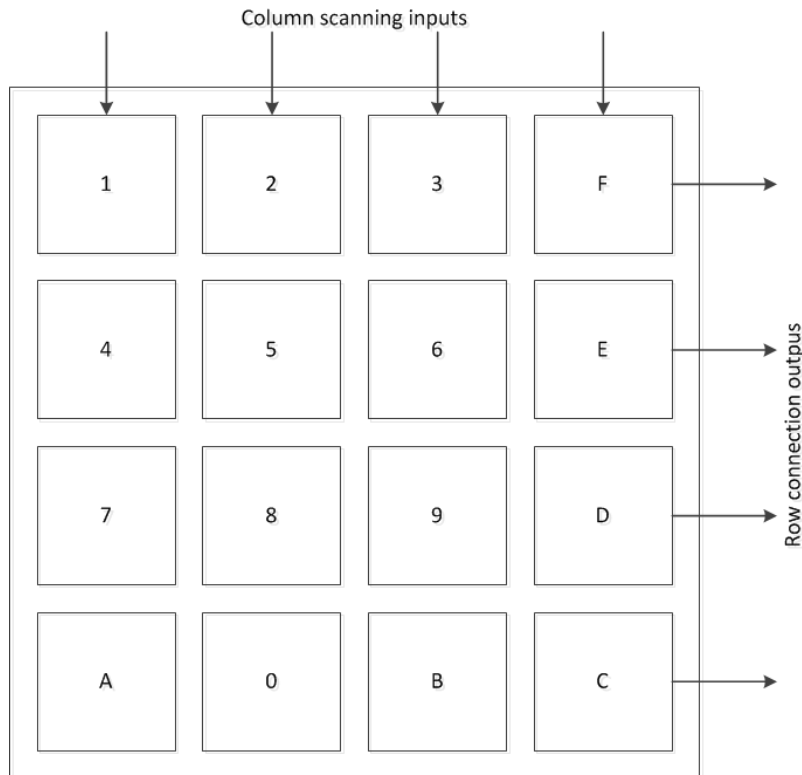

- Different to DIP switch and pushbutton, keypad provides coded inputs rather than raw on/off signal
- Assume no multiple key presses at the same time
- Questions:
 - How to handle variable numbers of input digits
 - How to differentiate numbers and operations
 - How to assign multiple roles to a single key


Mechanical switches

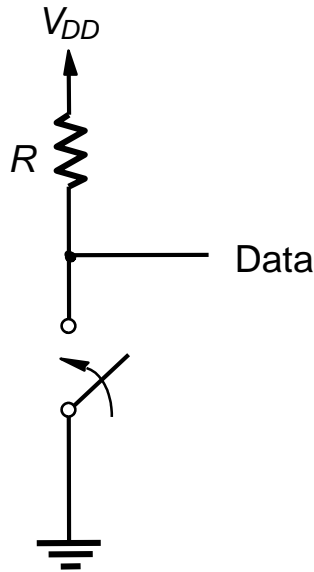




- If the switch is open, the *Data* signal = 1
- When the switch is now closed, it will bounce for some time, causing *Data* to oscillates between 1 and 0
- Bouncing persist for about 10 ms. Data alternates between 0 and 1, while you expect a clean signal
 - Lead into falsely recognised multiple presses
- Different mechanical devices may have different characteristics

Bouncing effect for DE0 pushbutton

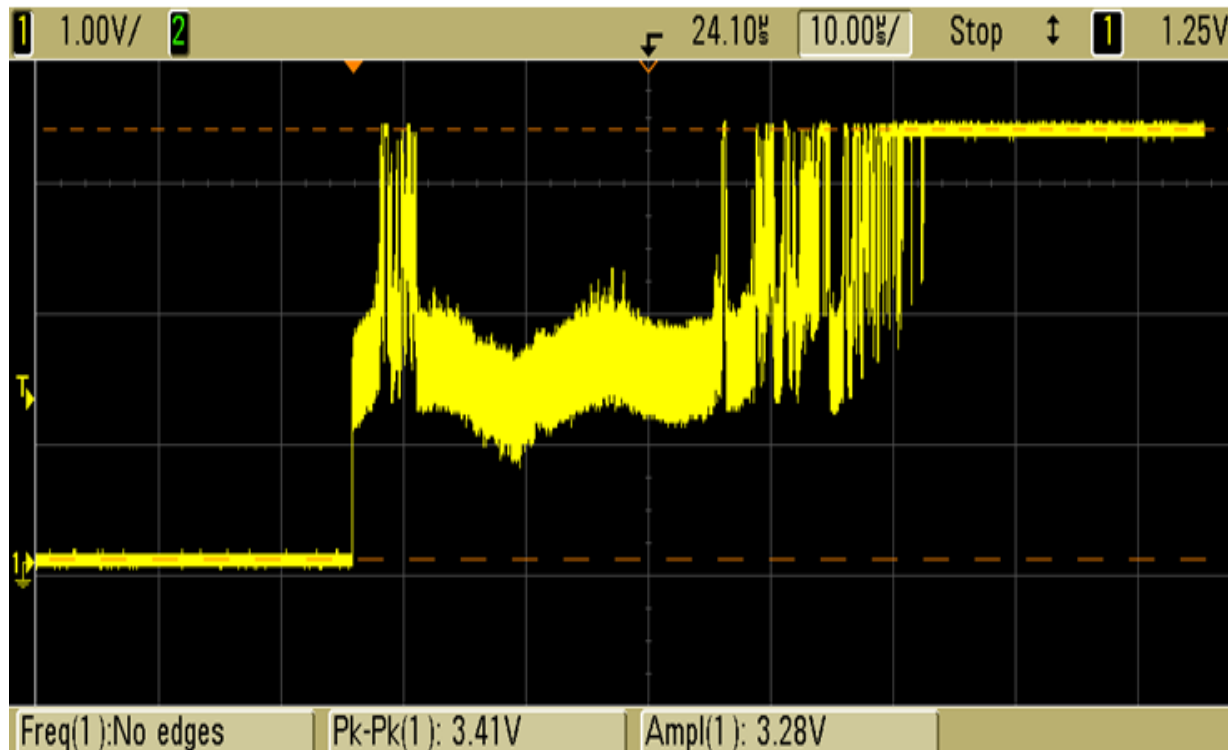
- Active low pushbutton
- Bouncing happens on the rising edge



Debouncer (cont'd)

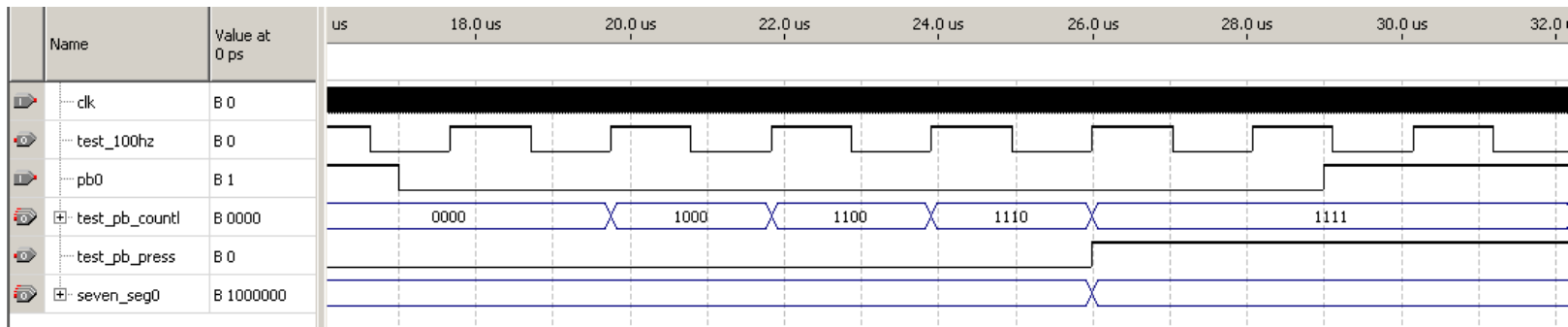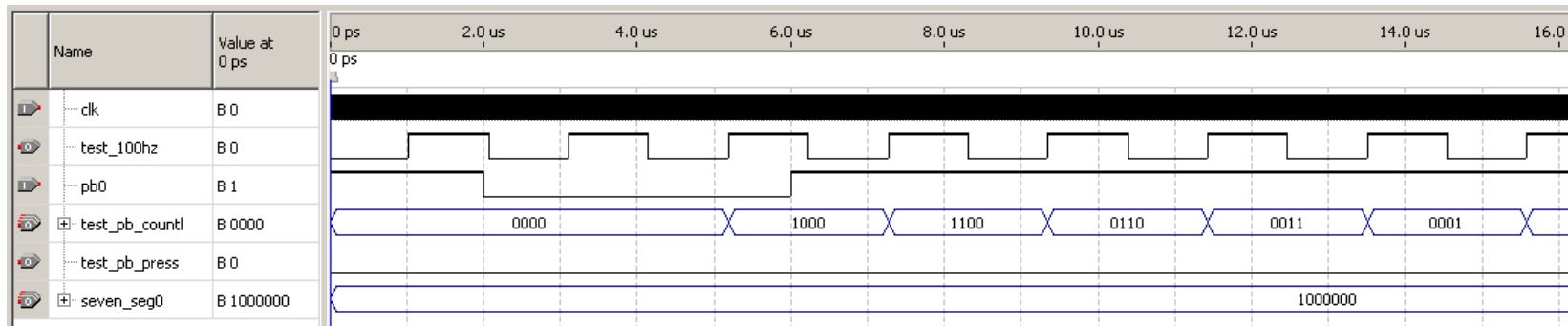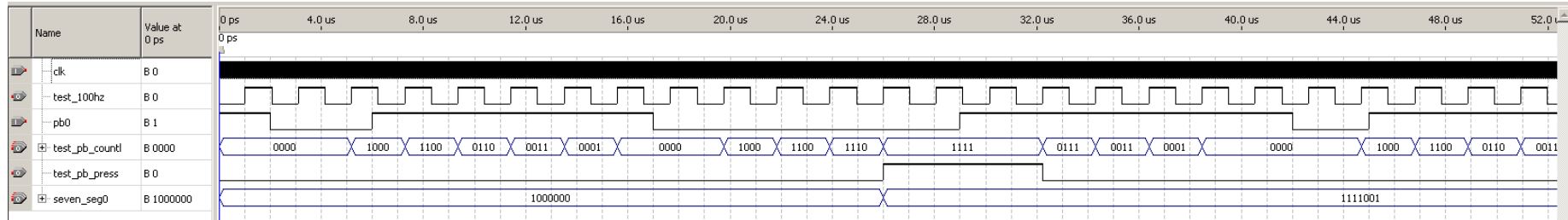


Debouncer (cont'd)

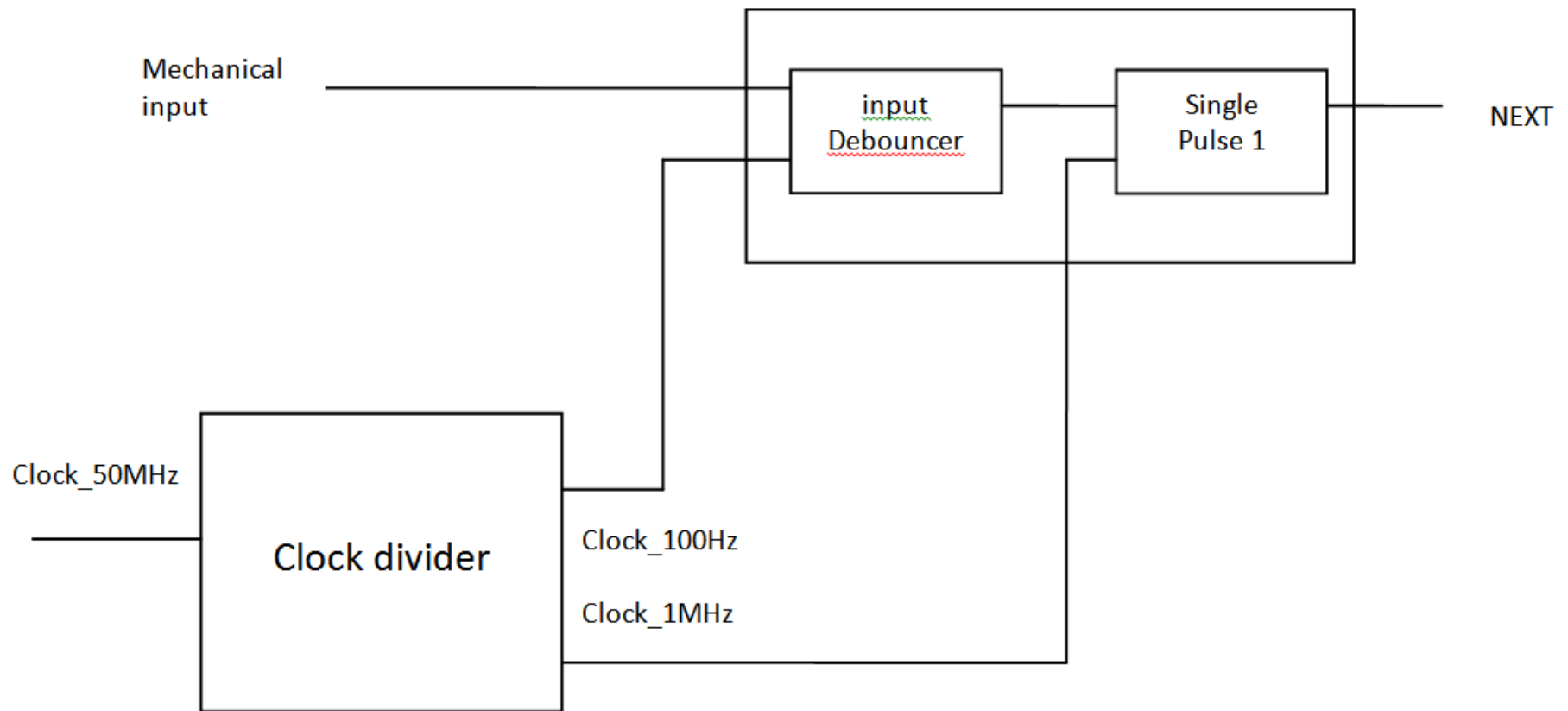

Control unit FSM

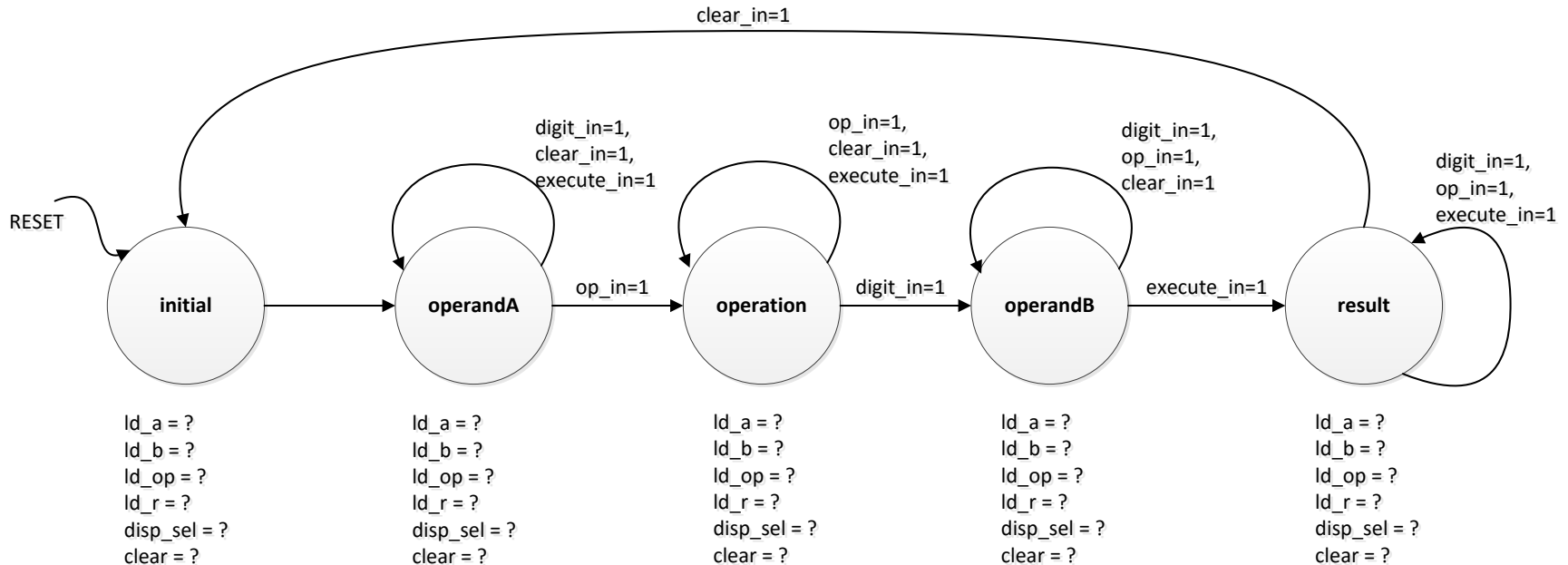- Who commands each individual component to reach harmonic overall operations



Register transfer action

Control signal	Register transfer	Comment
clear	$A \leftarrow 0, B \leftarrow 0, R \leftarrow 0, OP \leftarrow 0,$ $STATE \leftarrow INITIAL$	Initialize all registers to 0 and set FSM to the first state
ld_a	$A \leftarrow KEY_IN$	Load operand A
disp_sel=00 (A)	$DISPLAY \leftarrow A$	Display operand A it on 7-seg
ld_b	$B \leftarrow KEY_IN$	Load operand B
disp_sel=01 (B)	$DISPLAY \leftarrow B$	Display operand B on 7-seg
ld_op	$OP \leftarrow KEY_IN$	Load operation
ld_r, op_sel=op	$R \leftarrow A \text{ op } B$	Load result of selected operation
disp_sel=10 (R)	$DISPLAY \leftarrow R$	Display result on 7-seg

- FSM Design: in order to achieve the necessary register transfer actions, what control signals need to be outputted in each state?